

A sample diode RLC circuit

To get a feel for how to generate the MLN equations for a circuit that has both RLC and non-linear components, consider the circuit of fig. 1.1.

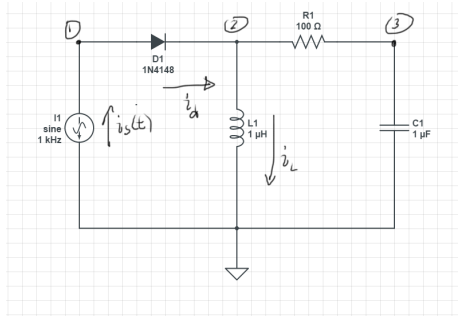


Figure 1.1: An RLC circuit with a diode.

The KCL equations for this circuit are

1. $0 = i_s - i_d$
2. $i_L + \frac{v_2 - v_3}{R} = i_d$
3. $\frac{v_3 - v_2}{R} + C \frac{dv_3}{dt} = 0$
4. $-v_2 + L \frac{di_L}{dt} = 0$
5. $i_d = I_0 \left(e^{(v_1 - v_2)/v_T} - 1 \right)$

With $Z = 1/R$, these can be put into the standard MLN matrix form as

$$\begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & Z & -Z & 1 \\ 0 & -Z & Z & 0 \\ 0 & -1 & 0 & 0 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ i_L \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & C & 0 \\ 0 & 0 & 0 & L \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ i_L \end{bmatrix}' = \begin{bmatrix} I_0 & 1 \\ -I_0 & 0 \\ 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} 1 \\ i_s(t) \end{bmatrix} + \begin{bmatrix} -I_0 \\ I_0 \\ 0 \\ 0 \end{bmatrix} \left[e^{(v_2 - v_3)/v_T} \right] \quad (1.1)$$

Let's write this as

$$\mathbf{G}\mathbf{X}(t) + \mathbf{C}\dot{\mathbf{X}}(t) = \mathbf{B}\mathbf{u}(t) + \mathbf{D}\mathbf{w}(t). \quad (1.2)$$

Here $\mathbf{u}(t)$ collects up all the unique signature sources (for example sources with each different frequency in the system), and $\mathbf{w}(t)$ is a vector of all the unique non-linear (time dependent) terms.

Assuming a bandwidth limited periodic source we know how to express any of the time dependent variables v_1, \dots in terms of their (discrete) Fourier transforms. Suppose that the Fourier coefficients for $v_a(t), u_b(t), w_c(t)$ are given by

$$\begin{aligned} v_a(t) &= \sum_{n=-N}^N V_n^{(a)} e^{j\omega_0 n t} \\ u_b(t) &= \sum_{n=-N}^N U_n^{(b)} e^{j\omega_0 n t} \\ w_c(t) &= \sum_{n=-N}^N W_n^{(c)} e^{j\omega_0 n t}. \end{aligned} \quad (1.3)$$

For example, in this circuit, if the source was zero phase signal at the fundamental frequency of our Fourier basis ($i_s(t) = e^{j\omega_0 t}$), the only non-zero Fourier components $U_n^{(a)}$ would be $U_0^{(1)} = 1, U_1^{(2)} = 1$.

First evaluating the derivatives, and then evaluating the result at each of the Nyquist times t_k , yields a $(2N + 1) \times 1$ equations

$$0 = \sum_{n=-N}^N e^{jn\omega_0 t_k} \left((\mathbf{G} + j\omega_0 n \mathbf{C}) \begin{bmatrix} V_n^{(1)} \\ V_n^{(2)} \\ \vdots \end{bmatrix} - \mathbf{B} \begin{bmatrix} U_n^{(1)} \\ U_n^{(2)} \end{bmatrix} - \mathbf{D} \begin{bmatrix} W_n^{(1)} \end{bmatrix} \right) \quad (1.4)$$

With the assumption of periodicity, each of these equations must separately equal zero for each (n, k) pair so that

$$(\mathbf{G} + j\omega_0 n \mathbf{C}) \begin{bmatrix} V_n^{(1)} \\ V_n^{(2)} \\ \vdots \end{bmatrix} = \mathbf{B} \begin{bmatrix} U_n^{(1)} \\ U_n^{(2)} \end{bmatrix} + \mathbf{D} \begin{bmatrix} W_n^{(1)} \end{bmatrix} \quad (1.5)$$

The next goal is to put this in block matrix form. First introducing discrete time sampling vectors

$$\mathbf{v}_a = \begin{bmatrix} v_a(t_{-N}) \\ v_a(t_{1-N}) \\ \vdots \\ v_a(t_{N-1}) \\ v_a(t_N) \end{bmatrix}, \quad \mathbf{u}_a = \begin{bmatrix} u_b(t_{-N}) \\ u_b(t_{1-N}) \\ \vdots \\ u_b(t_{N-1}) \\ u_b(t_N) \end{bmatrix}, \quad \mathbf{w}_a = \begin{bmatrix} w_c(t_{-N}) \\ w_c(t_{1-N}) \\ \vdots \\ w_c(t_{N-1}) \\ w_c(t_N) \end{bmatrix}, \quad (1.6)$$

and Fourier component vectors

$$\mathbf{V}_a = \begin{bmatrix} V_{-N}^{(a)} \\ V_{1-N}^{(a)} \\ \vdots \\ V_{N-1}^{(a)} \\ V_N^{(a)} \end{bmatrix}, \quad \mathbf{U}_b = \begin{bmatrix} U_{-N}^{(b)} \\ U_{1-N}^{(b)} \\ \vdots \\ U_{N-1}^{(b)} \\ U_N^{(b)} \end{bmatrix}, \quad \mathbf{W}_c = \begin{bmatrix} W_{-N}^{(c)} \\ W_{1-N}^{(c)} \\ \vdots \\ W_{N-1}^{(c)} \\ W_N^{(c)} \end{bmatrix}. \quad (1.7)$$

With $\alpha = e^{2\pi j/(2N+1)}$, and

$$\mathbf{F} = \begin{bmatrix} \alpha^{NN} & \alpha^{(N-1)N} & \dots & 1 & \dots & \alpha^{-(N-1)N} & \alpha^{-NN} \\ \alpha^{N(N-1)} & \alpha^{(N-1)(N-1)} & \dots & 1 & \dots & \alpha^{-(N-1)(N-1)} & \alpha^{-N(N-1)} \\ \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots \\ 1 & 1 & 1 & 1 & 1 & 1 & 1 \\ \vdots & \vdots & \vdots & \vdots & \vdots & \vdots & \vdots \\ \alpha^{-N(N-1)} & \alpha^{-(N-1)(N-1)} & \dots & 1 & \dots & \alpha^{N-1(N-1)} & \alpha^{N(N-1)} \\ \alpha^{-NN} & \alpha^{-NN} & \dots & 1 & \dots & \alpha^{(N-1)N} & \alpha^{NN} \end{bmatrix}, \quad (1.8)$$

in each case the time domain sampling vectors are related to the Fourier components by relations of the form

$$\mathbf{x} = \mathbf{F}\mathbf{X}. \quad (1.9)$$

1.1 Block matrix form, with physical parameter ordering

To understand how to put eq. (1.5) in block matrix form, it is helpful to consider a specific example. Consider again the specific example of the RLC circuit above, which has the form

$$\begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & Z & -Z & 1 \\ 0 & -Z & Z + j\omega_0 nC & 0 \\ 0 & -1 & 0 & +j\omega_0 nL \end{bmatrix} \begin{bmatrix} V_n^{(1)} \\ V_n^{(2)} \\ V_n^{(3)} \\ I_n^{(L)} \end{bmatrix} = \begin{bmatrix} I_n^{(1)} \\ I_n^{(2)} \\ I_n^{(3)} \\ I_n^{(4)} \end{bmatrix} \quad (1.10)$$

Here the $I^{(i)}$ terms are the DFT representations of both the linear and non-linear sources. Suppose for example that $N = 1$. One way to write eq. (1.10) would be

$$\begin{bmatrix} I_{-1}^{(1)} \\ I_0^{(1)} \\ I_1^{(1)} \\ I_{-1}^{(2)} \\ I_0^{(2)} \\ I_1^{(2)} \\ I_{-1}^{(3)} \\ I_0^{(3)} \\ I_1^{(3)} \\ I_{-1}^{(4)} \\ I_0^{(4)} \\ I_1^{(4)} \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ \hline 0 & 0 & 0 & Z & 0 & 0 & -Z & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & Z & 0 & 0 & -Z & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & Z & 0 & 0 & -Z & 0 & 0 & 1 \\ \hline 0 & 0 & 0 & -Z & 0 & 0 & Z & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -Z & 0 & 0 & Z & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & -Z & 0 & 0 & Z & 0 & 0 & 0 \\ \hline 0 & 0 & 0 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} V_{-1}^{(1)} \\ V_0^{(1)} \\ V_1^{(1)} \\ V_{-1}^{(2)} \\ V_0^{(2)} \\ V_1^{(2)} \\ V_{-1}^{(3)} \\ V_0^{(3)} \\ V_1^{(3)} \\ I_{-1}^{(L)} \\ I_0^{(L)} \\ I_1^{(L)} \end{bmatrix} + \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ \hline 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ \hline 0 & 0 & 0 & 0 & 0 & 0 & j\omega_0(-1)C & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & j\omega_0(0)C & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & j\omega_0(1)C & 0 & 0 & 0 \\ \hline 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & j\omega_0(-1)L & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & j\omega_0(0)L & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & j\omega_0(1)L \end{bmatrix} \begin{bmatrix} V_{-1}^{(1)} \\ V_0^{(1)} \\ V_1^{(1)} \\ V_{-1}^{(2)} \\ V_0^{(2)} \\ V_1^{(2)} \\ V_{-1}^{(3)} \\ V_0^{(3)} \\ V_1^{(3)} \\ I_{-1}^{(L)} \\ I_0^{(L)} \\ I_1^{(L)} \end{bmatrix} \quad (1.11)$$

With a vector of fourier coeffient vectors

$$\mathbf{V} = \begin{bmatrix} \mathbf{V}^{(1)} \\ \mathbf{V}^{(2)} \\ \mathbf{V}^{(3)} \\ \mathbf{I}^{(L)} \end{bmatrix}, \quad \mathbf{I} = \begin{bmatrix} \mathbf{I}^{(1)} \\ \mathbf{I}^{(2)} \\ \mathbf{I}^{(3)} \\ \mathbf{I}^{(4)} \end{bmatrix}. \quad (1.12)$$

and a $(2N + 1) \times (2N + 1)$ matrix of indexes

$$\mathbf{N} = \begin{bmatrix} -N & & & & \\ & 1 - N & & & \\ & & \ddots & & \\ & & & N - 1 & \\ & & & & N \end{bmatrix}, \quad (1.13)$$

1.3 Representing the linear sources

Assuming real sources with frequencies that are only multiples of the fundamental harmonic, a reasonable way to represent them in storage is with a pair of matrices

$$[\mathbf{I} \sim \mathbf{B}\boldsymbol{\omega}] . \quad (1.16)$$

If R is the dimension of \mathbf{G} and \mathbf{C} , then \mathbf{B} is a $R \times S$ dimension matrix, where S is the sum of

- 1, if there are any DC sources, plus
- 2 times the number of unique frequency sources.

For example, if there is a DC source and one AC source with frequency ν , then for column vectors \mathbf{b}_i this pair is of the form

$$\mathbf{U}\boldsymbol{\omega} = [\mathbf{b}_{-1} \quad \mathbf{b}_0 \quad \mathbf{b}_1] \begin{bmatrix} -2\pi\nu \\ 0 \\ 2\pi\nu \end{bmatrix} . \quad (1.17)$$

This representation produces the time domain representation exactly when there are only DC sources, and can be used to construct the Fourier coefficients by inspection when there are AC sources. For example, for $N = 1$ in the example above, the Fourier coefficient vector is

$$\mathbf{I} = \begin{bmatrix} \mathbf{b}_{-1} \\ \mathbf{b}_0 \\ \mathbf{b}_1 \end{bmatrix} . \quad (1.18)$$

If $N = 2$ was used, then we would have instead

$$\mathbf{I} = \begin{bmatrix} \mathbf{0} \\ \mathbf{b}_{-1} \\ \mathbf{b}_0 \\ \mathbf{b}_1 \\ \mathbf{0} \end{bmatrix} . \quad (1.19)$$

1.4 Representing non-linear sources

The time domain MNA eq. (1.2) include a wide range of matrix dimensions. It is now clear how to handle the transition to the frequency domain for all the linear terms. Working a simple diode example to understand how to handle the non-linear terms is useful. Consider the circuit of fig. 1.2.

With $Z = 1/R, Z_g = 1/R_g$, the KCL equations are

1. $(v_1 - v_2) Z_s = i_s - i_d$
2. $(v_2 - v_1) Z_s + v_2 Z_g = -i_s + i_d$

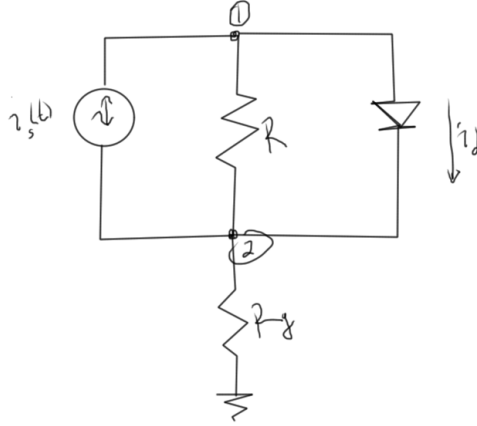


Figure 1.2: Simple diode circuit

Using the model $i_d = I^{(0)} \left(e^{(v_1 - v_2)/V_T} - 1 \right)$, with source $i_s = I^{(s)} \cos(\omega_0 t)$, this has the block matrix form

$$\mathbf{G} = \begin{bmatrix} Z_s & -Z_s \\ -Z_s & Z_s + Z_g \end{bmatrix}, \quad \mathbf{x} = \begin{bmatrix} v_1(t) \\ v_2(t) \end{bmatrix} \quad (1.20a)$$

$$\mathbf{B} = \begin{bmatrix} I^{(s)}/2 & -I^{(0)} & I^{(s)}/2 \\ -I^{(s)}/2 & I^{(0)} & -I^{(s)}/2 \end{bmatrix}, \quad \mathbf{u}(t) = \begin{bmatrix} e^{-j\omega_0 t} \\ 1 \\ e^{j\omega_0 t} \end{bmatrix} \quad (1.20b)$$

$$\mathbf{D} = \begin{bmatrix} I^{(0)} \\ -I^{(0)} \end{bmatrix}, \quad \mathbf{w}(t) = e^{(v_1(t) - v_2(t))/V_T}. \quad (1.20c)$$

If E_n is the nth DFT coefficient for $e(t) = e^{(v_1(t) - v_2(t))/V_T}$, then the DFT equations for the $N = 1$ DFT is

$$\begin{aligned} (V_{-1}^{(1)} - V_{-1}^{(2)}) Z_s &= I^{(s)}/2 - I^{(0)} E_{-1} \\ (V_{-1}^{(2)} - V_{-1}^{(1)}) Z_s + V_{-1}^{(2)} Z_g &= -I^{(s)}/2 + I^{(0)} E_{-1} \\ (V_0^{(1)} - V_0^{(2)}) Z_s &= I^{(0)} - I^{(0)} E_0 \\ (V_0^{(2)} - V_0^{(1)}) Z_s + V_0^{(2)} Z_g &= -I^{(0)} + I^{(0)} E_0 \\ (V_1^{(1)} - V_1^{(2)}) Z_s &= I^{(s)}/2 - I^{(0)} E_1 \\ (V_1^{(2)} - V_1^{(1)}) Z_s + V_1^{(2)} Z_g &= -I^{(s)}/2 + I^{(0)} E_1 \end{aligned} \quad (1.21)$$

Let $\mathbf{b} = [\mathbf{b}_{-1} \ \mathbf{b}_0 \ \mathbf{b}_1]$, and $\mathbf{D} = [\mathbf{d}_1]$. The block matrix equivalent form, by inspection, is

$$\begin{bmatrix} \mathbf{G} & 0 & 0 \\ 0 & \mathbf{G} & 0 \\ 0 & 0 & \mathbf{G} \end{bmatrix} \begin{bmatrix} V_{-1}^{(1)} \\ V_{-1}^{(2)} \\ V_0^{(1)} \\ V_0^{(2)} \\ V_1^{(1)} \\ V_1^{(2)} \end{bmatrix} = \begin{bmatrix} \mathbf{b}_{-1} \\ \mathbf{b}_0 \\ \mathbf{b}_1 \end{bmatrix} + \begin{bmatrix} \mathbf{d}_1 E_{-1} \\ \mathbf{d}_1 E_0 \\ \mathbf{d}_1 E_1 \end{bmatrix}. \quad (1.22)$$

This shows the stamping pattern required to form the non-linear portion of the Harmonic balance equations. The general pattern can be written as

$$\mathbf{YV} = \mathbf{I} + \mathcal{I}(\mathbf{V}), \quad (1.23)$$

Here \mathbf{Y} is block diagonal, and in general has blocks of $\mathbf{G} + j\omega_0 n \mathbf{C}$. The matrix \mathbf{I} was generated from the Fourier coefficients of all the linear sources, and $\mathcal{I}(\mathbf{V})$ encodes all the non-linear contributions to the system.

More general non-linear structure, for multiple diodes For the diode exponentials, these non-linear term will be of the form

$$\mathbf{Dw}(t) = \begin{bmatrix} \mathbf{d}_1 & \mathbf{d}_2 & \cdots & \mathbf{d}_S \end{bmatrix} \begin{bmatrix} w_1(t) \\ w_2(t) \\ \vdots \\ w_S(t) \end{bmatrix}, \quad (1.24)$$

where $w_i(t) = \exp((v_{i,1}(t) - v_{i,2}(t))/V_{T,i})$. If the DFT coordinates of these functions are $E_n^{(i)}$, then the frequency domain representation is

$$\mathcal{I}(\mathbf{V}) = \sum_{i=1}^S \begin{bmatrix} \mathbf{d}_i E_{-N}^{(i)} \\ \mathbf{d}_i E_{1-N}^{(i)} \\ \vdots \\ \mathbf{d}_i E_{N-1}^{(i)} \\ \mathbf{d}_i E_N^{(i)} \end{bmatrix}. \quad (1.25)$$

This is a $R(2N + 1) \times 1$ matrix, as expected.

The computation of these DFT coordinates is a bit messy since they are time dependent, and thus dependent on the (unknown) values of $V_n^{(1)}$. Consider the above circuit as an example where we have

$$w(t) = \exp((v_1(t) - v_2(t))/V_T). \quad (1.26)$$

The DFT inverse is

$$E_n = \sum_{k=-N}^N \exp((v_1(t_k) - v_2(t_k))/V_T) e^{-j\omega_0 n t_k}. \quad (1.27)$$

With $\mathbf{E} = (E_{-N}, E_{1-N}, \dots, E_{N-1}, E_N)$, this is

$$\begin{aligned} \mathbf{E} &= \frac{1}{2N+1} \bar{\mathbf{F}} \begin{bmatrix} \exp\left((v_{-N}^{(1)} - v_{-N}^{(2)})/v_T\right) \\ \exp\left((v_{1-N}^{(1)} - v_{1-N}^{(2)})/v_T\right) \\ \vdots \\ \exp\left((v_{N-1}^{(1)} - v_{N-1}^{(2)})/v_T\right) \\ \exp\left((v_N^{(1)} - v_N^{(2)})/v_T\right) \end{bmatrix} \\ &= \frac{1}{2N+1} \bar{\mathbf{F}} \begin{bmatrix} \exp\left([\mathbf{F}(\mathbf{V}^{(1)} - \mathbf{V}^{(2)})/v_T]_{-N}\right) \\ \exp\left([\mathbf{F}(\mathbf{V}^{(1)} - \mathbf{V}^{(2)})/v_T]_{1-N}\right) \\ \vdots \\ \exp\left([\mathbf{F}(\mathbf{V}^{(1)} - \mathbf{V}^{(2)})/v_T]_{N-1}\right) \\ \exp\left([\mathbf{F}(\mathbf{V}^{(1)} - \mathbf{V}^{(2)})/v_T]_N\right) \end{bmatrix}. \end{aligned} \quad (1.28)$$

With the introduction a term by term exponentiation operator

$$\exp[\mathbf{x}] = \begin{bmatrix} \exp(x_1) \\ \exp(x_2) \\ \vdots \end{bmatrix}, \quad (1.29)$$

this one Fourier coefficient vector is

$$\mathbf{E} = \frac{1}{2N+1} \bar{\mathbf{F}} \exp[\mathbf{F}(\mathbf{V}^{(1)} - \mathbf{V}^{(2)})/v_T]. \quad (1.30)$$

This is now completely expressed in terms of the unknown Fourier component vectors, each a subset of the aggregated ‘‘voltage’’, range selectable with the Matlab operation $\mathbf{V}^{(i)} = \mathbf{V}(i : R : \text{end})$.

1.5 Newton’s method

In order to solve the system, Newton’s method on the Fourier coefficients is required. Solutions to $\mathcal{F}(\mathbf{V}) = 0$ are sought, where

$$\mathcal{F}(\mathbf{V}) = \mathbf{Y}\mathbf{V} - \mathbf{I} - \mathcal{I}(\mathbf{V}). \quad (1.31)$$

Here the sources current vector DFT coordinates have been split into the linear contributions \mathbf{I} and nonlinear contributions \mathcal{I} defined by eq. (1.25).

Working with ones-indexed coordinates of $\mathbf{V} = [V_k]_k$, where $k \in [1, R(2N+1)]$, the Jacobian is

$$\mathbf{J} = \mathbf{Y} - [\partial \mathcal{I}_r / \partial V_s]_{rs}. \quad (1.32)$$

To calculate these partials we need the partials of the coordinates of \mathbf{E} of eq. (1.30). The k th coordinate of $\mathbf{V}^{(1)}, \mathbf{V}^{(2)}$ in terms of the coordinates of the $R(2N+1)$ vector of unknowns \mathbf{V} are

$$\begin{aligned} [\mathbf{V}^{(1)}]_k &= V_{1+(k-1)R} \\ [\mathbf{V}^{(2)}]_k &= V_{2+(k-1)R} \end{aligned} \quad (1.33)$$

Using summation convention, with sums over any repeated indexes implied, those coordinates are

$$E_r = \frac{1}{2N+1} \bar{F}_{ra} \exp(F_{ab}(V_{1+(b-1)R} - V_{2+(b-1)R})/v_T). \quad (1.34)$$

The partials now follow immediately

$$\frac{\partial E_r}{\partial V_s} = \frac{1}{2N+1} \frac{1}{v_T} \bar{F}_{ra} F_{ab} \exp(F_{ab}(V_{1+(b-1)R} - V_{2+(b-1)R})/v_T) (\delta_{s,1+(b-1)R} - \delta_{s,2+(b-1)R}). \quad (1.35)$$

Generalization To generalize this, suppose that the diode exponential was associated with voltages spanning nodes m, n so that

$$\mathbf{E} = \frac{1}{2N+1} \bar{\mathbf{F}} \exp[\mathbf{F}(\mathbf{V}^{(m)} - \mathbf{V}^{(n)})/v_T]. \quad (1.36)$$

In this case, the coordinates of the physical “voltages” are

$$\begin{aligned} [\mathbf{V}^{(m)}]_k &= V_{m+(k-1)R} \\ [\mathbf{V}^{(n)}]_k &= V_{n+(k-1)R} \end{aligned} \quad (1.37)$$

so

$$E_r = \frac{1}{2N+1} \bar{F}_{ra} \exp(F_{ab}(V_{m+(b-1)R} - V_{n+(b-1)R})/v_T). \quad (1.38)$$

The Jacobian partials are

$$\frac{\partial E_r}{\partial V_s} = \frac{1}{2N+1} \frac{1}{v_T} \bar{F}_{ra} F_{ab} \exp(F_{ab}(V_{m+(b-1)R} - V_{n+(b-1)R})/v_T) (\delta_{s,m+(b-1)R} - \delta_{s,n+(b-1)R}). \quad (1.39)$$

Note that this Jacobian

$$\mathbf{J}_{\mathbf{E}} = \left[\frac{\partial E_r}{\partial V_s} \right]_{rs} \quad (1.40)$$

is a $(2N+1) \times R(2N+1)$ matrix.

The full Jacobian of $\mathcal{I}(\mathbf{V})$ is

$$\mathbf{J}_{\mathcal{I}}(\mathbf{V}) = \sum_{i=1}^S \begin{bmatrix} \mathbf{d}_i \frac{\partial E_{-N}^{(i)}}{\partial \mathbf{V}} \\ \mathbf{d}_i \frac{\partial E_{1-N}^{(i)}}{\partial \mathbf{V}} \\ \vdots \\ \mathbf{d}_i \frac{\partial E_{N-1}^{(i)}}{\partial \mathbf{V}} \\ \mathbf{d}_i \frac{\partial E_N^{(i)}}{\partial \mathbf{V}} \end{bmatrix}. \quad (1.41)$$

Where $\partial E_k^{(i)}/\partial \mathbf{V}$ is the k th row of $\mathbf{J}_{E^{(i)}}$. The complete Jacobian is

$$\mathbf{J} = \mathbf{Y} - \mathbf{J}_I(\mathbf{V}). \quad (1.42)$$

1.6 A matrix formulation of Harmonic Balance non-linear currents

Because it was simple, a coordinate expansion of the Jacobian of the non-linear currents was good to get a feeling for the structure of the equations. However, a Jacobian of that form is impossibly slow to compute for larger N . It seems plausible that eliminating the coordinate expansion, expressing both the current and the Jacobian directly in terms of the Harmonic Balance unknowns vector \mathbf{V} , would lead to a simpler set of equations that could be implemented in a computationally more effective way.

To aid in this discovery, consider the simple RC load diode circuit of fig. 1.3. It's not too hard to start from scratch with the time domain nodal equations for this circuit, which are

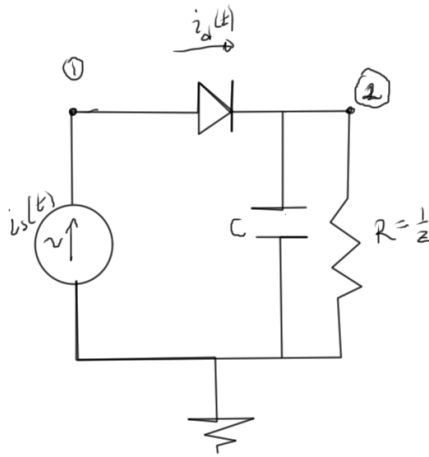


Figure 1.3: Simple diode and resistor circuit

1. $0 = i_s - i_d$
2. $Zv^{(2)} + Cdv^{(2)}/dt = i_d$
3. $i_d = I_0 \left(e^{(v^{(1)} - v^{(2)})/V_T} - 1 \right)$

To setup for matrix form, let

$$\mathbf{v}(t) = \begin{bmatrix} v^{(1)}(t) \\ v^{(2)}(t) \end{bmatrix} \quad (1.43a)$$

$$\mathbf{G} = \begin{bmatrix} 0 & 0 \\ 0 & Z \end{bmatrix} \quad (1.43b)$$

$$\mathbf{C} = \begin{bmatrix} 0 & 0 \\ 0 & C \end{bmatrix} \quad (1.43c)$$

$$\mathbf{d} = \begin{bmatrix} 1 \\ -1 \end{bmatrix} \quad (1.43d)$$

$$\mathbf{b} = \begin{bmatrix} 1 \\ 0 \end{bmatrix}, \quad (1.43e)$$

so that the time domain equations can be written as

$$\begin{aligned} \mathbf{G}\mathbf{v}(t) + \mathbf{C}\mathbf{v}'(t) &= \mathbf{b}i_s(t) + I_0\mathbf{d} \left(e^{(v^{(1)}(t)-v^{(2)}(t))/V_T} - 1 \right) \\ &= [\mathbf{b} \quad -I_0\mathbf{d}] \begin{bmatrix} i_s(t) \\ 1 \end{bmatrix} + I_0\mathbf{d}e^{(v^{(1)}(t)-v^{(2)}(t))/V_T}. \end{aligned} \quad (1.44)$$

Harmonic Balance is essentially the assumption that the input and outputs are assumed to be a bandwidth limited periodic signal, and the non-linear components can be approximated by the same

$$i_s(t) = \sum_{n=-N}^N I_n^{(s)} e^{j\omega_0 n t}, \quad (1.45a)$$

$$v^{(k)}(t) = \sum_{n=-N}^N V_n^{(k)} e^{j\omega_0 n t}, \quad (1.45b)$$

$$\epsilon(t) = e^{(v^{(1)}(t)-v^{(2)}(t))/V_T} \simeq \sum_{n=-N}^N E_n e^{j\omega_0 n t}, \quad (1.45c)$$

The approximation in eq. (1.45c) is an equality only at the Nyquist sampling times $t_k = Tk/(2N+1)$. The Fourier series provides a periodic extension to other times that will approximate the underlying periodic non-linear relation.

With all the time dependence locked into the exponentials, the derivatives are really easy to calculate

$$\frac{d}{dt}v^{(k)}(t) = \sum_{n=-N}^N j\omega_0 n V_n^{(k)} e^{j\omega_0 n t}. \quad (1.46)$$

Inserting all of these into eq. (1.44) gives

$$\sum_{n=-N}^N e^{j\omega_0 n t} (\mathbf{G} + j\omega_0 n \mathbf{C}) \begin{bmatrix} V_n^{(1)} \\ V_n^{(2)} \end{bmatrix} = \sum_{n=-N}^N e^{j\omega_0 n t} \left(-I_0\mathbf{d}\delta_{n0} + \mathbf{b}I_n^{(s)} + I_0\mathbf{d}E_n \right). \quad (1.47)$$

The periodic assumption requires equality for each $e^{j\omega_0 n t}$, or

$$(\mathbf{G} + j\omega_0 n \mathbf{C}) \begin{bmatrix} V_n^{(1)} \\ V_n^{(2)} \end{bmatrix} = -I_0\mathbf{d}\delta_{n0} + \mathbf{b}I_n^{(s)} + I_0\mathbf{d}E_n. \quad (1.48)$$

For illustration, consider the $N = 1$ case, where the block matrix form is

$$\begin{bmatrix} \mathbf{G} + j\omega_0(-1)\mathbf{C} & 0 & 0 \\ 0 & \mathbf{G} + j\omega_0(0)\mathbf{C} & 0 \\ 0 & 0 & \mathbf{G} + j\omega_0(1)\mathbf{C} \end{bmatrix} \begin{bmatrix} V_{-1}^{(1)} \\ V_{-1}^{(2)} \\ V_0^{(1)} \\ V_0^{(2)} \\ V_1^{(1)} \\ V_1^{(2)} \end{bmatrix} = \begin{bmatrix} \mathbf{b}I_{-1}^{(s)} \\ \mathbf{b}I_0^{(s)} - I_0\mathbf{d} \\ \mathbf{b}I_1^{(s)} \end{bmatrix} + I_0 \begin{bmatrix} \mathbf{d}E_{-1} \\ \mathbf{d}E_0 \\ \mathbf{d}E_1 \end{bmatrix}. \quad (1.49)$$

The structure of this equation is

$$\mathbf{Y}\mathbf{V} = \mathbf{I} + \mathcal{I}(\mathbf{V}), \quad (1.50)$$

The non-linear current $\mathcal{I}(\mathbf{V})$ needs to be examined further. How much of this can be precomputed, and what is the simplest way to compute the Jacobian?

With

$$\mathbf{E} = \begin{bmatrix} E_{-1} \\ E_0 \\ E_1 \end{bmatrix}, \quad \boldsymbol{\epsilon} = \begin{bmatrix} \epsilon_{-1} \\ \epsilon_0 \\ \epsilon_1 \end{bmatrix}, \quad (1.51)$$

the non-linear current is

$$\begin{aligned} \mathcal{I} &= I_0 \begin{bmatrix} \mathbf{d}E_{-1} \\ \mathbf{d}E_0 \\ \mathbf{d}E_1 \end{bmatrix} \\ &= I_0 \begin{bmatrix} \mathbf{d} \begin{bmatrix} 1 & 0 & 0 \end{bmatrix} \mathbf{E} \\ \mathbf{d} \begin{bmatrix} 0 & 1 & 0 \end{bmatrix} \mathbf{E} \\ \mathbf{d} \begin{bmatrix} 0 & 0 & 1 \end{bmatrix} \mathbf{E} \end{bmatrix} \\ &= I_0 \begin{bmatrix} \mathbf{d} & 0 & 0 \\ 0 & \mathbf{d} & 0 \\ 0 & 0 & \mathbf{d} \end{bmatrix} \mathbf{F}^{-1}\boldsymbol{\epsilon} \end{aligned} \quad (1.52)$$

In the last step $\mathbf{E} = \mathbf{F}^{-1}\boldsymbol{\epsilon}$ has been factored out (in its inverse Fourier form). With

$$\mathbf{D} = \begin{bmatrix} \mathbf{d} & 0 & 0 \\ 0 & \mathbf{d} & 0 \\ 0 & 0 & \mathbf{d} \end{bmatrix}, \quad (1.53)$$

the current is

$$\mathcal{I}(\mathbf{V}) = I_0 \mathbf{D} \mathbf{F}^{-1} \boldsymbol{\epsilon}(\mathbf{V}). \quad (1.54)$$

The next step is finding an appropriate form for $\boldsymbol{\epsilon}$

$$\begin{aligned}
\boldsymbol{\epsilon} &= \begin{bmatrix} \epsilon(t_{-1}) \\ \epsilon(t_0) \\ \epsilon(t_1) \end{bmatrix} \\
&= \begin{bmatrix} \exp\left(\left(v_{-1}^{(1)} - v_{-1}^{(2)}\right)/V_T\right) \\ \exp\left(\left(v_0^{(1)} - v_0^{(2)}\right)/V_T\right) \\ \exp\left(\left(v_1^{(1)} - v_1^{(2)}\right)/V_T\right) \end{bmatrix} \\
&= \begin{bmatrix} \exp\left(\begin{bmatrix} 1 & 0 & 0 \end{bmatrix} \left(\mathbf{v}^{(1)} - \mathbf{v}^{(2)}\right)/V_T\right) \\ \exp\left(\begin{bmatrix} 0 & 1 & 0 \end{bmatrix} \left(\mathbf{v}^{(1)} - \mathbf{v}^{(2)}\right)/V_T\right) \\ \exp\left(\begin{bmatrix} 0 & 0 & 1 \end{bmatrix} \left(\mathbf{v}^{(1)} - \mathbf{v}^{(2)}\right)/V_T\right) \end{bmatrix} \\
&= \begin{bmatrix} \exp\left(\begin{bmatrix} 1 & 0 & 0 \end{bmatrix} \mathbf{F} \left(\mathbf{V}^{(1)} - \mathbf{V}^{(2)}\right)/V_T\right) \\ \exp\left(\begin{bmatrix} 0 & 1 & 0 \end{bmatrix} \mathbf{F} \left(\mathbf{V}^{(1)} - \mathbf{V}^{(2)}\right)/V_T\right) \\ \exp\left(\begin{bmatrix} 0 & 0 & 1 \end{bmatrix} \mathbf{F} \left(\mathbf{V}^{(1)} - \mathbf{V}^{(2)}\right)/V_T\right) \end{bmatrix}.
\end{aligned} \tag{1.55}$$

It would be nice to have the difference of frequency domain vectors expressed in terms of \mathbf{V} , which can be done with a bit of rearrangement

$$\begin{aligned}
\mathbf{V}^{(1)} - \mathbf{V}^{(2)} &= \begin{bmatrix} V_{-1}^{(1)} - V_{-1}^{(2)} \\ V_0^{(1)} - V_0^{(2)} \\ V_1^{(1)} - V_1^{(2)} \end{bmatrix} \\
&= \begin{bmatrix} 1 & -1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & -1 \end{bmatrix} \begin{bmatrix} V_{-1}^{(1)} \\ V_{-1}^{(2)} \\ V_0^{(1)} \\ V_0^{(2)} \\ V_1^{(1)} \\ V_1^{(2)} \end{bmatrix} \\
&= \begin{bmatrix} \mathbf{d}^T & 0 & 0 \\ 0 & \mathbf{d}^T & 0 \\ 0 & 0 & \mathbf{d}^T \end{bmatrix} \mathbf{V} \\
&= \mathbf{D}^T \mathbf{V},
\end{aligned} \tag{1.56}$$

$$\mathbf{H} = \mathbf{F} \mathbf{D}^T / V_T = \begin{bmatrix} \mathbf{h}_1^T \\ \mathbf{h}_2^T \\ \mathbf{h}_3^T \end{bmatrix}, \tag{1.57}$$

which allows the non-linear current to can now be completely expressed in terms of \mathbf{V} .

$$\boxed{\boldsymbol{\epsilon}(\mathbf{V}) = \begin{bmatrix} e^{\mathbf{h}_1^T \mathbf{V}} \\ e^{\mathbf{h}_2^T \mathbf{V}} \\ e^{\mathbf{h}_3^T \mathbf{V}} \end{bmatrix}}. \tag{1.58}$$

Jacobian With a compact matrix representation of the non-linear current, attention can now be turned to the Jacobian of the non-linear current. Let $\mathbf{A} = I_0 \mathbf{D}\mathbf{F}^{-1} = [a_{ij}]_{ij}$, the current (with summation implied) is

$$\mathcal{I} = [a_{ik}\epsilon_k], \quad (1.59)$$

with coordinates

$$\begin{aligned} \mathcal{I}_i &= a_{ik}\epsilon_k \\ &= a_{ik} \exp(\mathbf{h}_k^T \mathbf{V}). \end{aligned} \quad (1.60)$$

so the Jacobian components are

$$\begin{aligned} [\mathbf{J}^{\mathcal{I}}]_{ij} &= a_{ik}\epsilon_k \\ &= a_{ik} \frac{\partial}{\partial V_j} \exp(\mathbf{h}_k^T \mathbf{V}) \\ &= a_{ik} h_{kj} \exp(\mathbf{h}_k^T \mathbf{V}). \end{aligned} \quad (1.61)$$

Factoring out $\mathbf{U} = [h_{ij} \exp(\mathbf{h}_i^T \mathbf{V})]_{ij}$,

$$\begin{aligned} \mathbf{J}^{\mathcal{I}} &= \mathbf{A}\mathbf{U} \\ &= \mathbf{A} \begin{bmatrix} [h_{11} & h_{12} & \cdots & h_{1,R(2N+1)}] \exp(\mathbf{h}_1^T \mathbf{V}) \\ [h_{21} & h_{22} & \cdots & h_{2,R(2N+1)}] \exp(\mathbf{h}_2^T \mathbf{V}) \\ [h_{31} & h_{32} & \cdots & h_{3,R(2N+1)}] \exp(\mathbf{h}_3^T \mathbf{V}) \end{bmatrix} \\ &= \mathbf{A} \begin{bmatrix} \mathbf{h}_1^T \exp(\mathbf{h}_1^T \mathbf{V}) \\ \mathbf{h}_2^T \exp(\mathbf{h}_2^T \mathbf{V}) \\ \mathbf{h}_3^T \exp(\mathbf{h}_3^T \mathbf{V}) \end{bmatrix}. \end{aligned} \quad (1.62)$$

A quick sanity check of dimensions seems worthwhile, and shows that all is well

- $\mathbf{A} : R(2N+1) \times 2N+1$
- $\mathbf{U} : 2N+1 \times R(2N+1)$
- $\mathbf{J}^{\mathcal{I}} : R(2N+1) \times R(2N+1)$

The Jacobian of the non-linear current is now completely determined

$$\mathbf{J}^{\mathcal{I}}(\mathbf{V}) = I_0 \mathbf{D}\mathbf{F}^{-1} \begin{bmatrix} \mathbf{h}_1^T \exp(\mathbf{h}_1^T \mathbf{V}) \\ \mathbf{h}_2^T \exp(\mathbf{h}_2^T \mathbf{V}) \\ \mathbf{h}_3^T \exp(\mathbf{h}_3^T \mathbf{V}) \end{bmatrix}. \quad (1.63)$$

Newton's method solution All the pieces required for a Newton's method solution are now in place. The goal is to find a value of \mathbf{V} that provides the zero

$$f(\mathbf{V}) = \mathbf{Y}\mathbf{V} - \mathbf{I} - \mathcal{I}(\mathbf{V}). \quad (1.64)$$

Expansion to first order around an initial guess \mathbf{V}^0 , gives

$$f(\mathbf{V}^0 + \Delta\mathbf{V}) = f(\mathbf{V}^0) + \mathbf{J}(\mathbf{V}^0)\Delta\mathbf{V} \approx 0, \quad (1.65)$$

where the full Jacobian of $f(\mathbf{V})$ is

$$\mathbf{J}(\mathbf{V}) = \mathbf{Y} - \mathbf{J}^{\mathcal{I}}(\mathbf{V}). \quad (1.66)$$

The Newton's method refinement of the initial guess follows by inversion

$$\Delta\mathbf{V} = - \left(\mathbf{Y} - \mathbf{J}^{\mathcal{I}}(\mathbf{V}^0) \right)^{-1} f(\mathbf{V}^0). \quad (1.67)$$

Bibliography

- [1] Franco Giannini and Giorgio Leuzzi. *Nonlinear Microwave Circuit Design*. Wiley Online Library, 2004. 1.2