

ECE1254H Modeling of Multiphysics Systems. Lecture 3: Nodal Analysis. Taught by Prof. Piero Triverio

1.1 Disclaimer

Peeter's lecture notes from class. These may be incoherent and rough.

1.2 Nodal Analysis

Avoiding branch currents can reduce the scope of the computational problem. Consider the same circuit fig. 1.1, this time introducing only node voltages as unknowns

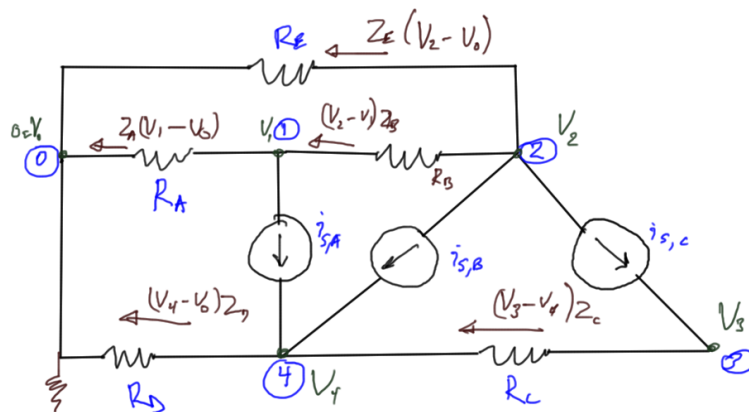


Figure 1.1: Resistive circuit with current sources

Unknowns: node voltages: V_1, V_2, \dots, V_4
Equations are KCL at each node except 0.

1. $\frac{V_1-0}{R_A} + \frac{V_1-V_2}{R_B} + i_{S,A} = 0$
2. $\frac{V_2-0}{R_E} + \frac{V_2-V_1}{R_B} + i_{S,B} + i_{S,C} = 0$

$$3. \frac{V_3 - V_4}{R_C} - i_{S,C} = 0$$

$$4. \frac{V_4 - 0}{R_D} + \frac{V_4 - V_3}{R_C} - i_{S,A} - i_{S,B} = 0$$

In matrix form this is

$$\begin{bmatrix} \frac{1}{R_A} + \frac{1}{R_B} & -\frac{1}{R_B} & 0 & 0 \\ -\frac{1}{R_B} & \frac{1}{R_B} + \frac{1}{R_E} & 0 & 0 \\ 0 & 0 & \frac{1}{R_C} & -\frac{1}{R_C} \\ 0 & 0 & -\frac{1}{R_C} & \frac{1}{R_C} + \frac{1}{R_D} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \\ V_4 \end{bmatrix} = \begin{bmatrix} -i_{S,A} \\ -i_{S,B} - i_{S,C} \\ i_{S,C} \\ i_{S,A} + i_{S,B} \end{bmatrix} \quad (1.1)$$

Introducing the nodal matrix G , we write this as

$$G\bar{V}_N = \bar{I}_S \quad (1.2)$$

We identify the stamp for a resistor of value R between nodes n_1 and n_2

$$\begin{matrix} & n_1 & n_2 \\ n_1 & \left[\begin{array}{cc} \frac{1}{R} & -\frac{1}{R} \\ -\frac{1}{R} & \frac{1}{R} \end{array} \right] \\ n_2 & \end{matrix} \quad (1.3)$$

where we have a set of rows and columns for each of the node voltages n_1, n_2 .

Note that some care is required to use this nodal analysis method since we required the invertible relationship $i = V/R$. We also cannot handle short circuits $V = 0$, or voltage sources $V = 5$ (say). We will also have trouble with differential terms like inductors.

Recap of node branch equations We had

- KCL: $A \cdot \bar{I}_B = \bar{I}_S$
- Constitutive: $\bar{I}_B = \alpha A^T \bar{V}_N$,

- Nodal equations: $\overset{G}{\boxed{A\alpha A^T}} \bar{V}_N = \bar{I}_S$

where \bar{I}_B was the branch currents, A was the incidence matrix, and $\alpha = \begin{bmatrix} \frac{1}{R_1} & & & \\ & \frac{1}{R_2} & & \\ & & \ddots & \end{bmatrix}$.

The stamp can be observed in the multiplication of the contribution for a single resistor, where we see that the incidence matrix has the form $G = A\alpha A^T$

$$\begin{aligned}
 G &= \begin{matrix} & \downarrow \\ n_1 & \begin{bmatrix} +1 \\ -1 \end{bmatrix} \\ n_2 & \end{matrix} \left[\begin{array}{c} \frac{1}{R} \end{array} \right] \begin{matrix} n_1 & n_2 \\ +1 & -1 \end{matrix} \\
 &= \begin{matrix} n_1 & n_2 \\ n_2 & n_1 \end{matrix} \begin{bmatrix} \frac{1}{R} & -\frac{1}{R} \\ -\frac{1}{R} & \frac{1}{R} \end{bmatrix}
 \end{aligned} \tag{1.4}$$

Theoretical facts Noting that $(AB)^T = B^T A^T$, it is clear that the nodal matrix $G = A\alpha A^T$ is symmetric

$$\begin{aligned}
 G^T &= (A\alpha A^T)^T \\
 &= (A^T)^T \alpha^T A^T \\
 &= A\alpha A^T \\
 &= G
 \end{aligned} \tag{1.5}$$

1.3 Modified nodal analysis (MNA)

This is the method that we find in software such as spice.

To illustrate the method, consider the same circuit, augmented with an additional voltage sources as in fig. 1.2.

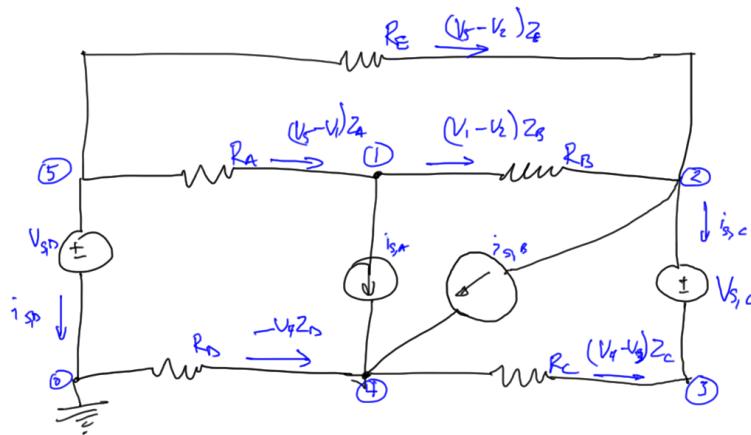


Figure 1.2: Resistive circuit with current and voltage sources

We know wish to have the following unknowns

- node voltages $(N - 1)$: V_1, V_2, \dots, V_5

- branch currents for selected components (K): $i_{S,C}, i_{S,D}$

We will have two less unknowns for this system than with standard nodal analysis. Our equations are

1. $-\frac{V_5-V_1}{R_A} + \frac{V_1-V_2}{R_B} + i_{S,A} = 0$
2. $\frac{V_2-V_5}{R_E} + \frac{V_2-V_1}{R_B} + i_{S,B} + i_{S,C} = 0$
3. $-i_{S,C} + \frac{V_3-V_4}{R_C} = 0$
4. $\frac{V_4-0}{R_D} + \frac{V_4-V_3}{R_C} - i_{S,A} - i_{S,B} = 0$
5. $\frac{V_5-V_2}{R_E} + \frac{V_5-V_1}{R_A} + i_{S,D} = 0$

Put into giant matrix form, this is

$$\begin{array}{c} G \\ -A_V^T \end{array} \left[\begin{array}{ccccc|c} Z_A + Z_B & -Z_B & \cdot & \cdot & -Z_A & -1 \\ -Z_B & Z_B - Z_E & \cdot & \cdot & -Z_E & +1 \\ \cdot & \cdot & Z_C & -Z_C & \cdot & \\ \cdot & \cdot & -Z_C & Z_C + Z_D & \cdot & \\ -Z_A & -Z_E & & & Z_A + Z_E & -1 \\ \hline & +1 & -1 & & & 1 \end{array} \right] \begin{array}{c} A_V \\ \left[\begin{array}{c} V_1 \\ V_2 \\ V_3 \\ V_4 \\ V_5 \\ i_{S,C} \\ i_{S,D} \end{array} \right] \end{array} = \begin{array}{c} \left[\begin{array}{c} -i_{S,A} \\ -i_{S,B} \\ 0 \\ i_{S,A} + i_{S,B} \\ 0 \\ V_{S,C} \\ V_{S,D} \end{array} \right] \end{array} \quad (1.6)$$

Call the extension to the nodal matrix G , the voltage incidence matrix A_V .